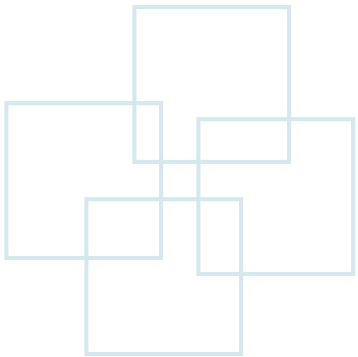



Class 12

State Machine






State Machine

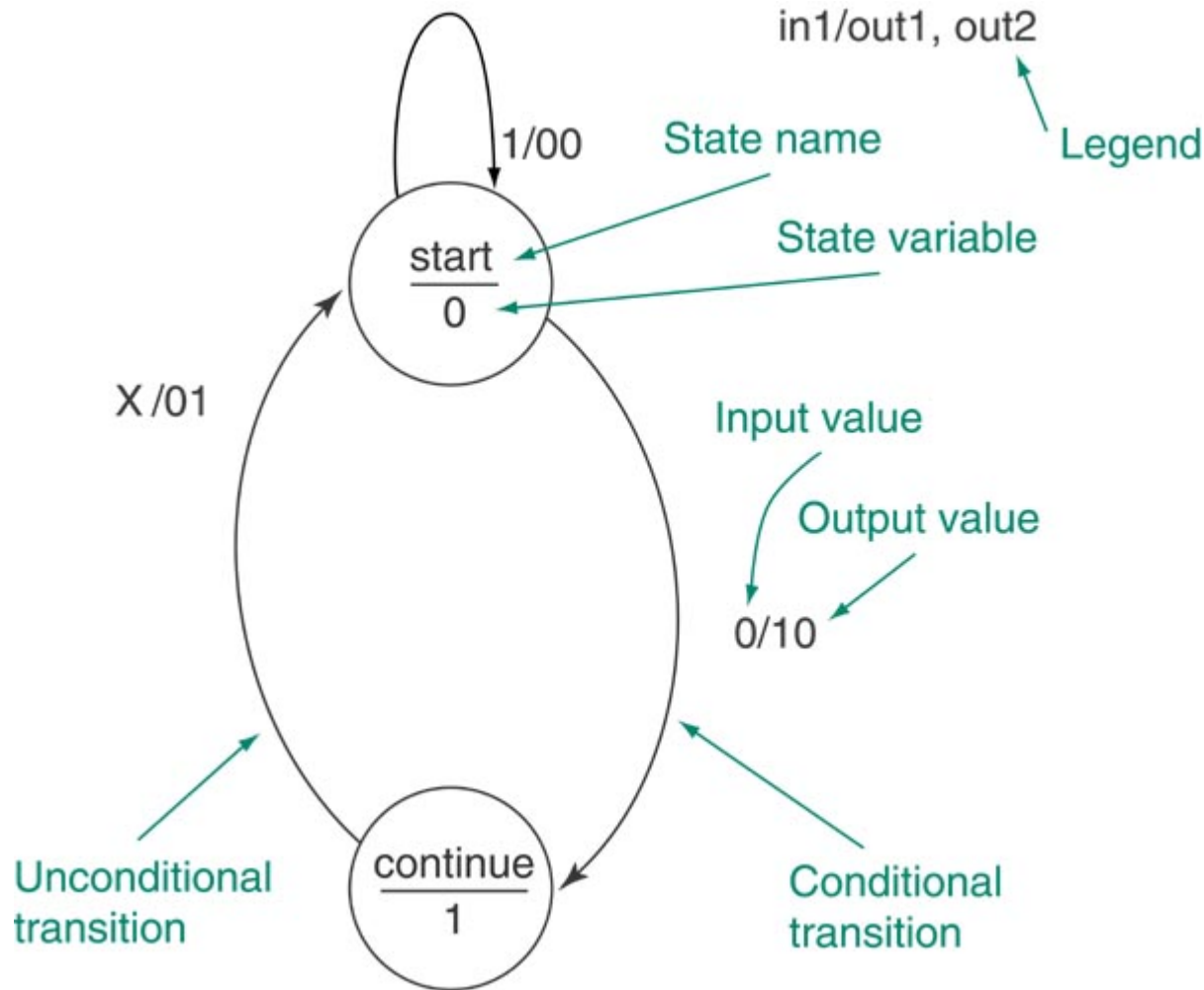



Unused States in State Machines

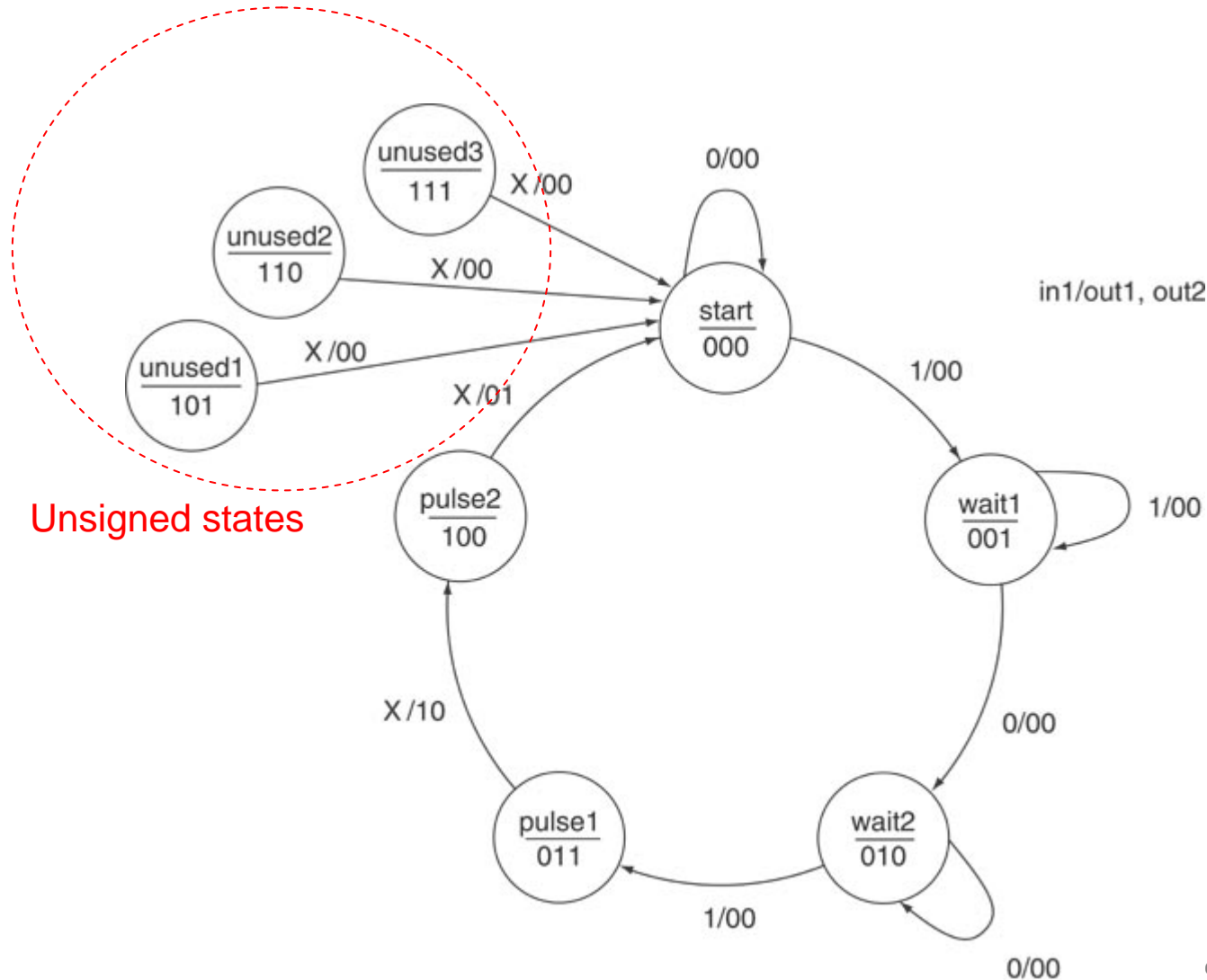



State Machine (Cont.)

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY sngl_pls IS
  PORT(
    clk, sync: IN STD_LOGIC;
    pulse: OUT STD_LOGIC);
END sngl_pls;

ARCHITECTURE pulser OF sngl_pls IS
  TYPE PULSE_STATE IS (seek, find);
  SIGNAL status: PULSE_STATE;
BEGIN
  PROCESS (clk)
  BEGIN


```

```

IF (clk'EVENT and clk = '1') THEN
  CASE status IS
    WHEN seek =>
      IF (sync = '1') THEN
        status <= seek;
        pulse <= '0';
      ELSE
        status <= find;
        pulse <= '1';
      END IF;
    WHEN find =>
      IF (sync = '1') THEN
        status <= seek;
        pulse <= '0';
      ELSE
        status <= find;
        pulse <= '0';
      END IF;
  END CASE;
END IF;
END PROCESS;
END pulser;

```

Type enumeration

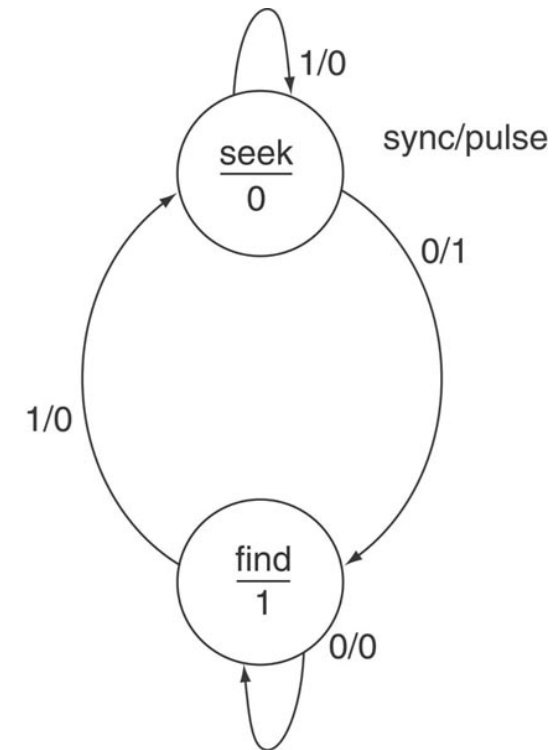



Push Button Debouncer

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
```

```
ENTITY pbdebouncer IS
  PORT(
    clk, pb2: IN STD_LOGIC;
    Hex0: OUT STD_LOGIC_VECTOR(0 to 7));
END pbdebouncer;
```

Define constants to debounce 5ms

```
ARCHITECTURE a OF pbdebouncer IS
  CONSTANT TicksPerMilliSecond: INTEGER := 50000;
  CONSTANT DebounceTime: INTEGER := TicksPerMilliSecond*5;
  SIGNAL PressedTime: NATURAL := 0;
  SIGNAL cnt: NATURAL RANGE 0 to 9;
```

```
BEGIN
  PROCESS (clk)
  BEGIN
    -- Change the shifting rate
    IF (clk'EVENT and clk = '1') THEN
      IF (pb2='0') THEN -- Push button is pressed
        IF (PressedTime < DebounceTime) THEN -- Wait for debounce time
          PressedTime <= PressedTime + 1;
        ELSIF (PressedTime = DebounceTime) THEN -- Debounce time is reached
          PressedTime <= DebounceTime + 1; -- stop counting
```

```
          cnt <= cnt + 1;
          IF (cnt >= 9) THEN
            cnt <= 0;
          END IF;
```

Equals to:

- $cnt \leq (cnt + 1) \bmod 10;$
- $cnt - (cnt / 10) * 10;$

```
        END IF;
      ELSE
        PressedTime <= 0;
      END IF;
    END IF;
```


Push button is not pressed

hexadecimal

```
-- Display the counter
CASE cnt IS
  WHEN 0 => Hex0 <= x"03"; -- 0
  WHEN 1 => Hex0 <= x"9F"; -- 1
  WHEN 2 => Hex0 <= x"25"; -- 2
  WHEN 3 => Hex0 <= x"0D"; -- 3
  WHEN 4 => Hex0 <= x"99"; -- 4
  WHEN 5 => Hex0 <= x"49"; -- 5
  WHEN 6 => Hex0 <= x"C1"; -- 6
  WHEN 7 => Hex0 <= x"1F"; -- 7
  WHEN 8 => Hex0 <= x"01"; -- 8
  WHEN 9 => Hex0 <= x"19"; -- 9
  WHEN others => Hex0 <= x"FF"; -- blank
END CASE;
END PROCESS;
END a;
```



Traffic Light

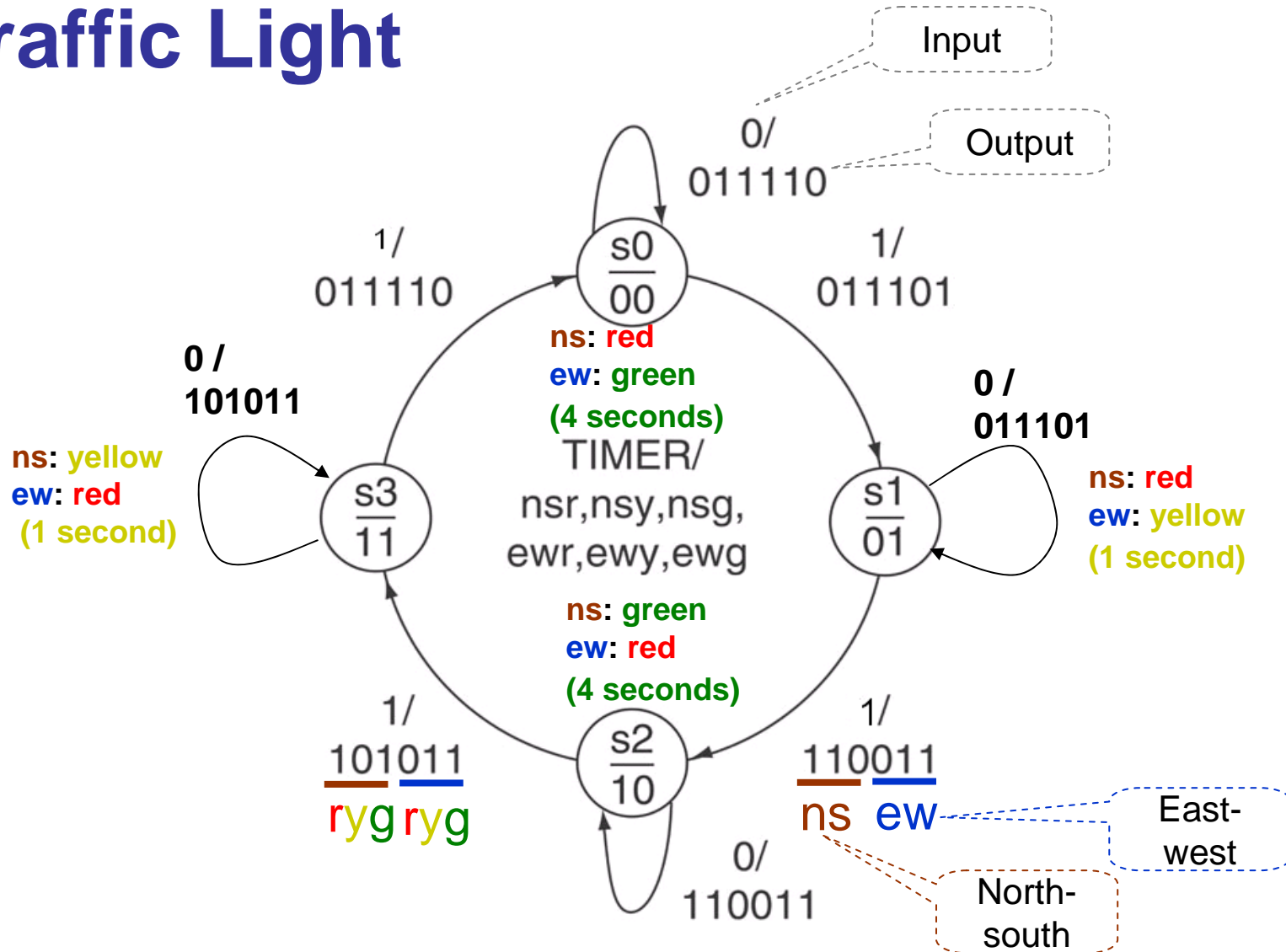




Lab 12

- Design a counter with a push button debouncer
 - Implement a two-digit counter that counts from 0 to 99.
 - Hex1 shows the digit of 10s, and hex0 shows the digit of 1s.
 - When PushButton2 is pressed the 2-digit counter is advanced by 1.
- Design a traffic light
 - Red light time is 5s, green light time is 4s, and yellow light time is 1s.
 - Hex3(/Hex2) is on to show the remaining time of the red light of the north-south (/west-east) direction; otherwise, Hex3 (/Hex2) is off.
 - Initial state: s0

| LED ₉ | LED ₈ | LED ₇ | LED ₂ | LED ₁ | LED ₀ |
|------------------|------------------|------------------|------------------|------------------|------------------|
| ns | ns | ns | ew | ew | ew |
| Red | Yellow | Green | Red | Yellow | Green |
| Hex3 | | | Hex2 | | |

Traffic Light


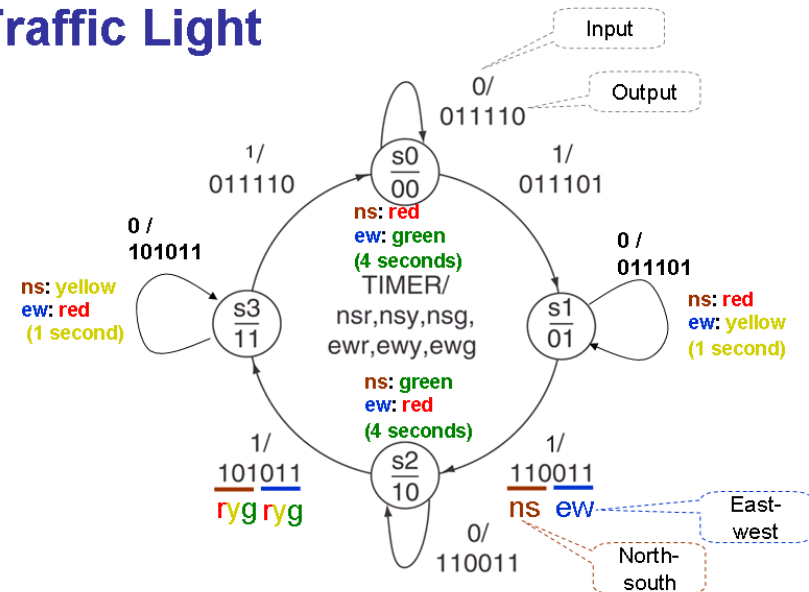


• Report:

- Write down what you have learned from this lab. (實驗心得)



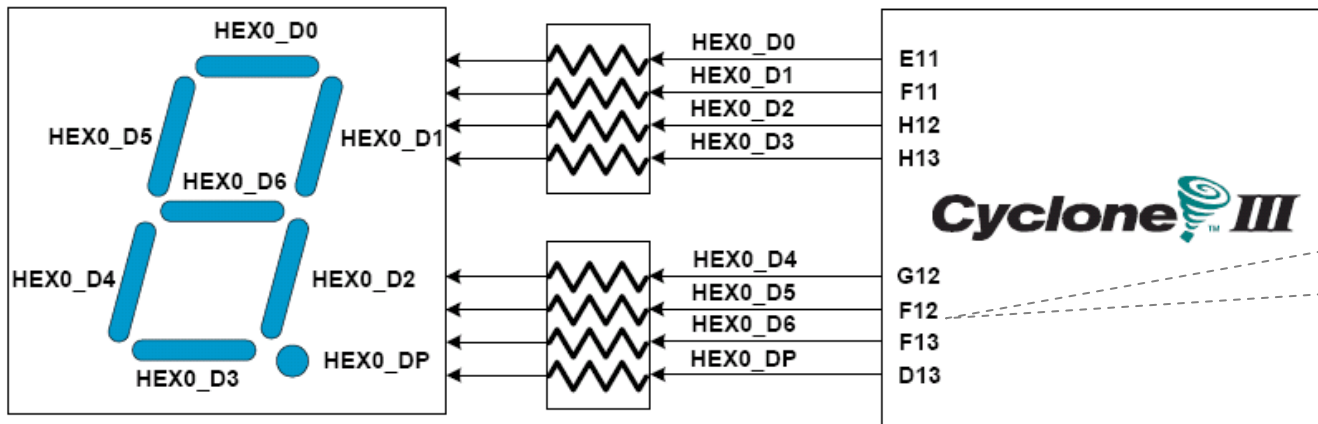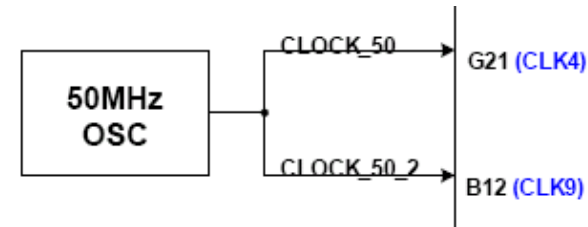7-Segment Displays & DE0 – External Clock



Pin number
(active-low)

| Signal Name | FPGA Pin No. |
|-------------|--------------|
|-------------|--------------|

| | |
|-----------|---------|
| HEX0_D[0] | PIN_E11 |
| HEX0_D[1] | PIN_F11 |
| HEX0_D[2] | PIN_H12 |
| HEX0_D[3] | PIN_H13 |
| HEX0_D[4] | PIN_G12 |
| HEX0_D[5] | PIN_F12 |
| HEX0_D[6] | PIN_F13 |
| HEX0_DP | PIN_D13 |

| | |
|-----------|---------|
| HEX1_D[0] | PIN_A13 |
| HEX1_D[1] | PIN_B13 |
| HEX1_D[2] | PIN_C13 |
| HEX1_D[3] | PIN_A14 |
| HEX1_D[4] | PIN_B14 |
| HEX1_D[5] | PIN_E14 |
| HEX1_D[6] | PIN_A15 |
| HEX1_DP | PIN_B15 |



| | |
|-----------|---------|
| HEX2_D[0] | PIN_D15 |
| HEX2_D[1] | PIN_A16 |
| HEX2_D[2] | PIN_B16 |
| HEX2_D[3] | PIN_E15 |
| HEX2_D[4] | PIN_A17 |
| HEX2_D[5] | PIN_B17 |
| HEX2_D[6] | PIN_F14 |
| HEX2_DP | PIN_A18 |

| | |
|-----------|---------|
| HEX3_D[0] | PIN_B18 |
| HEX3_D[1] | PIN_F15 |
| HEX3_D[2] | PIN_A19 |
| HEX3_D[3] | PIN_B19 |
| HEX3_D[4] | PIN_C19 |
| HEX3_D[5] | PIN_D19 |
| HEX3_D[6] | PIN_G15 |
| HEX3_DP | PIN_G16 |



Pushbutton and Slide Switches

Pin number

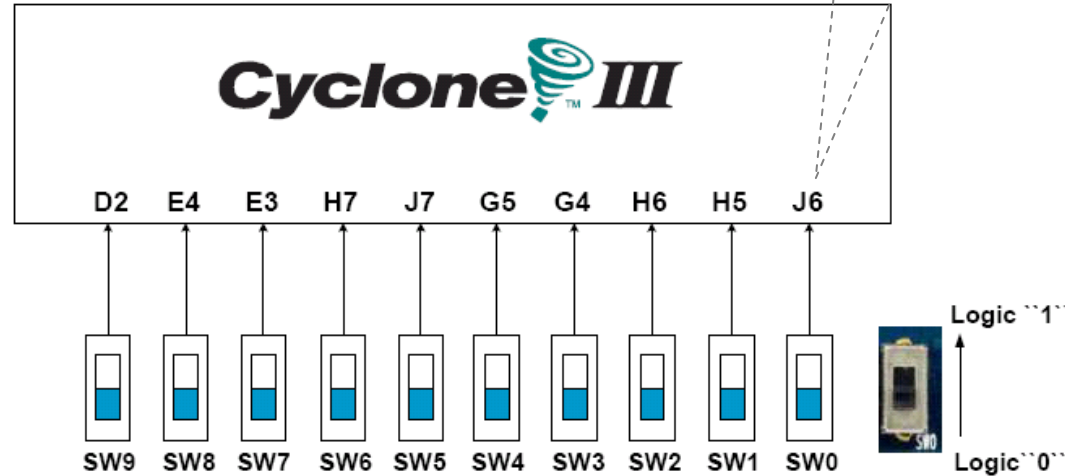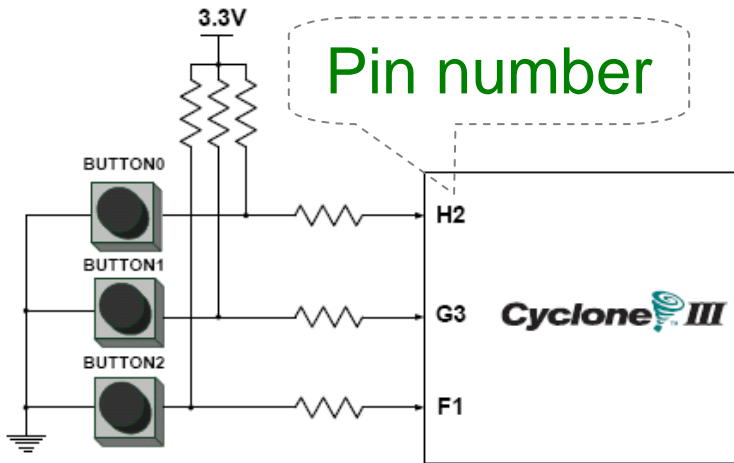

3 Pushbutton switches:
 Not pressed → Logic High
 Pressed → Logic Low


| Signal Name | FPGA Pin No. |
|-------------|--------------|
| BUTTON [0] | PIN_ H2 |
| BUTTON [1] | PIN_ G3 |
| BUTTON [2] | PIN_ F1 |

10 Slide switches (Sliders):
 Up → Logic High
 Down → Logic

| | | | |
|-------|--------|-------|--------|
| SW[0] | PIN_J6 | SW[5] | PIN_J7 |
| SW[1] | PIN_H5 | SW[6] | PIN_H7 |
| SW[2] | PIN_H6 | SW[7] | PIN_E3 |
| SW[3] | PIN_G4 | SW[8] | PIN_E4 |
| SW[4] | PIN_G5 | SW[9] | PIN_D2 |



LEDs

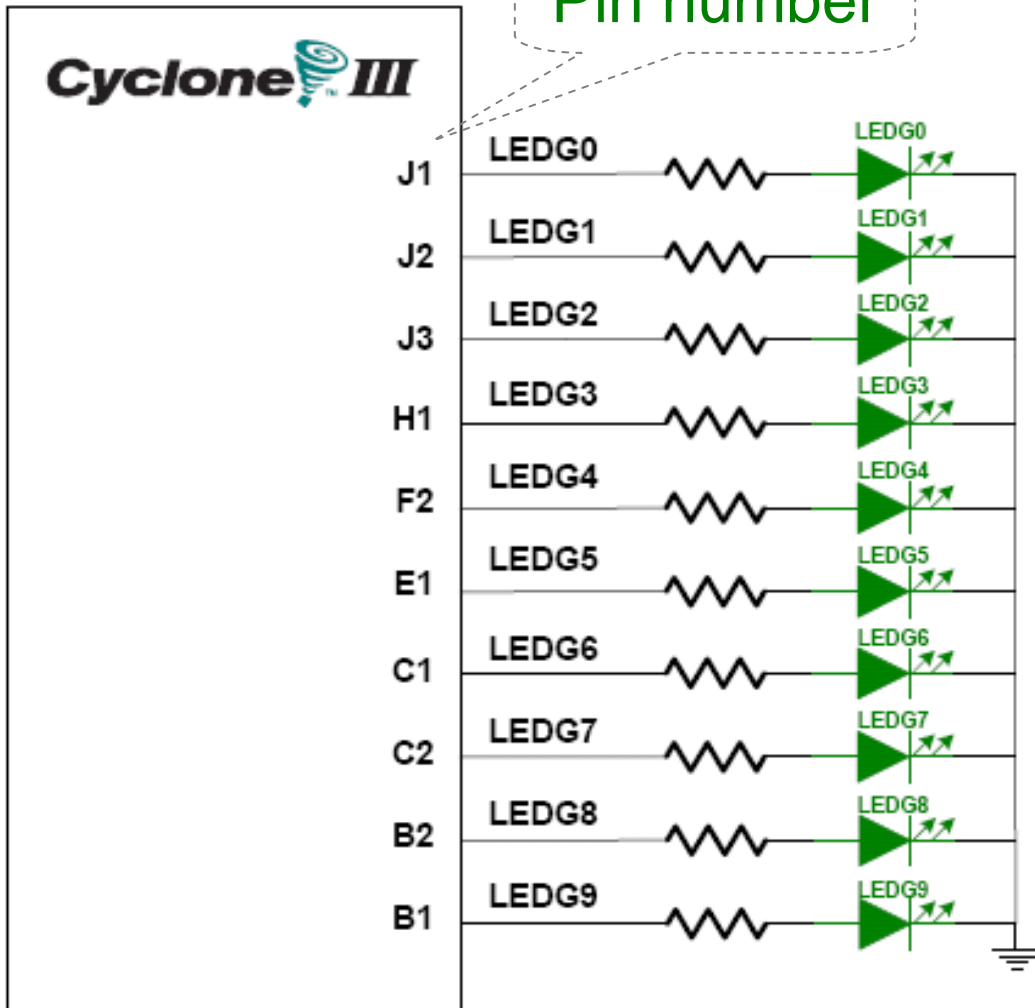

10 LEDs
 Output high → LED on
 Output low → LED off

| Signal Name | FPGA Pin No. |
|-------------|--------------|
| LEDG[0] | PIN_J1 |
| LEDG[1] | PIN_J2 |
| LEDG[2] | PIN_J3 |
| LEDG[3] | PIN_H1 |
| LEDG[4] | PIN_F2 |
| LEDG[5] | PIN_E1 |
| LEDG[6] | PIN_C1 |
| LEDG[7] | PIN_C2 |
| LEDG[8] | PIN_B2 |
| LEDG[9] | PIN_B1 |