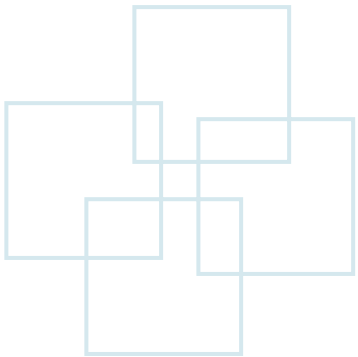


# Class 13


# Memory





 
# Memory

- A memory is a digital device or circuit that can store one or more bits of data.
- The simplest memory device is a **D-type latch** or a **D flip-flop**.




data\_in:  
8-bit data  
input

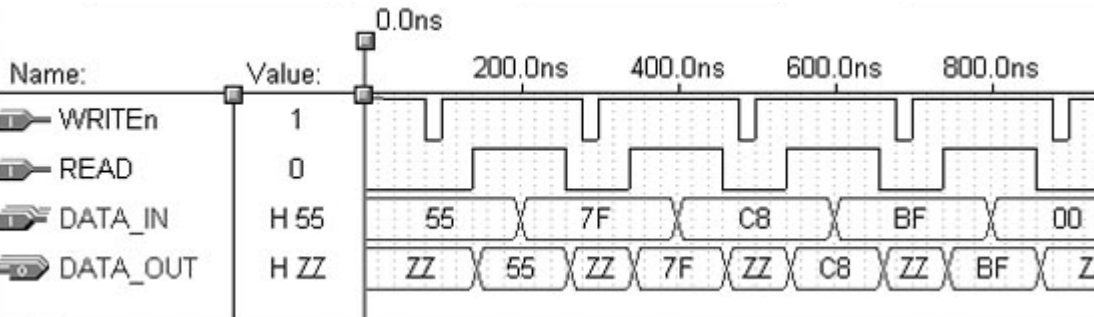

Input gate enable  
(Write)


Output enable  
(Read)

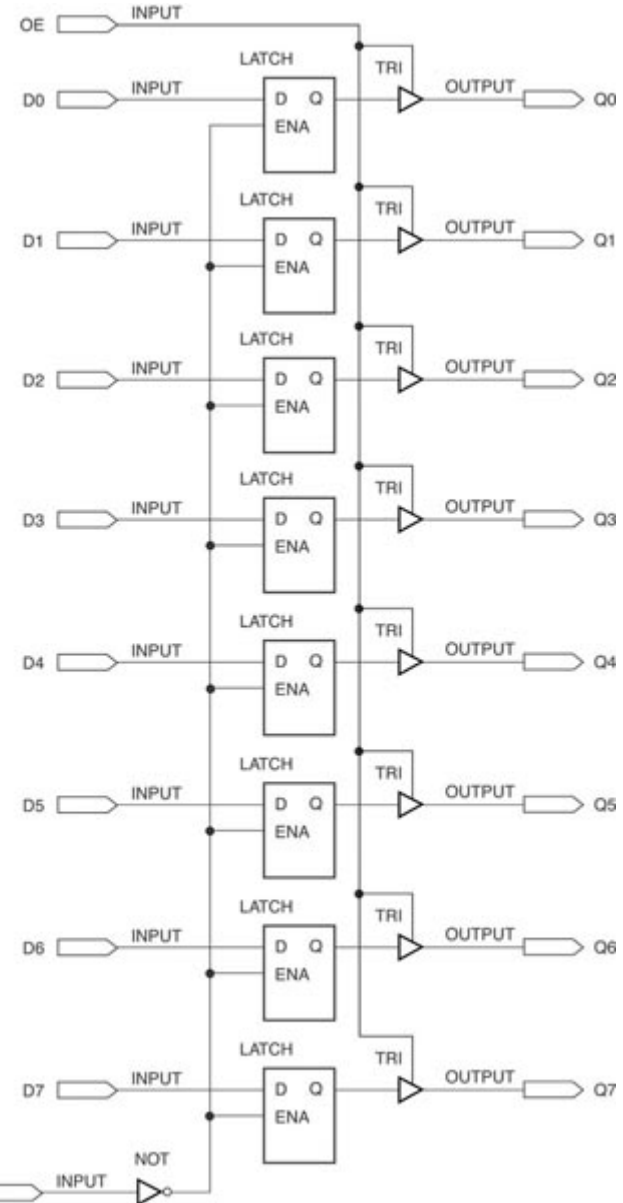



# 8-Bit Latch


Output enable  
(Read)

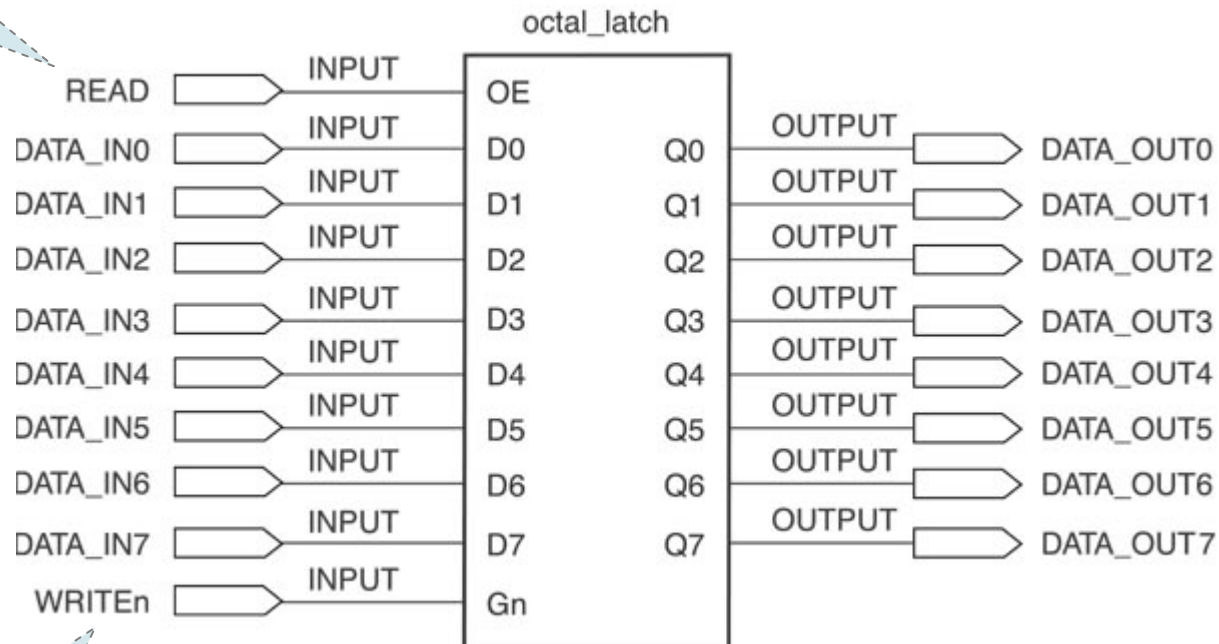

Input gate enable  
(Write)



# Address and Data Lines

 

a. Address and data lines

$D_8$		$D_1$	
1	0	1	1
0	0	0	1
1	1	0	1
0	0	0	0
0	1	1	1
1	0	0	0
0	1	0	1
1	0	1	1
1	0	1	0
0	1	0	1
1	1	0	1
0	0	0	1
1	1	0	0
1	1	0	1
1	1	1	1

b. Contents (data) and location (address)

Addresses				
Binary				
Hexadecimal				
0	0000	0000	0000	0000
0	0000	0000	0001	0001
0	0000	0000	0010	0002
0	0000	0000	0011	0003
0	0000	0000	0100	0004
0	0000	0000	0101	0005
0	0000	0000	0110	0006
⋮				⋮
1	1111	1111	1101	1FFD
1	1111	1111	1110	1FFE
1	1111	1111	1111	1FFF


**8K x 8 Memory**  
 Address:  $2^{13} = 8192$  WORD  
 Data: 8 bits (= 1 WORD)

$addr(0) = "10110101"$ , when  $A_{12} \dots A_0 = 000000000000 = 0x000$   
 $addr(1) = "00011011"$ , when  $A_{12} \dots A_0 = 000000000001 = 0x001$



# Address, Data, and Control Signals

Address lines

 


a. 1K x 4 RAM

Low: Write  
High: Read

Output enable


Chip enable

 

b. 1K x 8 ROM (EPROM)



# Memory Control Signals

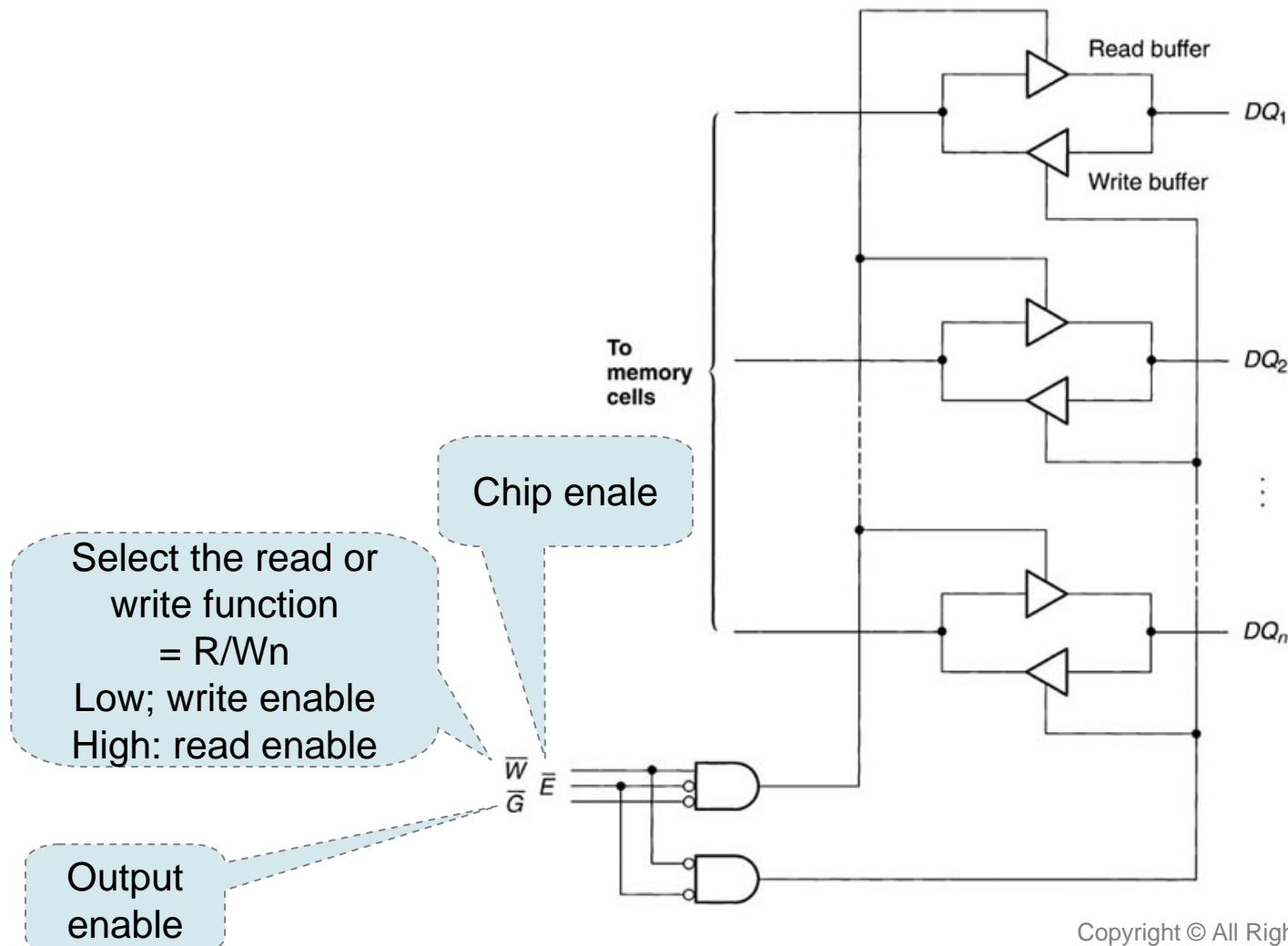



# 4x8bit Memory - Behavioral Design

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;
USE ieee.std_logic_arith.all;

```

```

ENTITY Memory IS
PORT(
  SlideSwitch: IN STD_LOGIC_VECTOR(9 downto 0);
  PushButton: IN STD_LOGIC_VECTOR(2 downto 0);
  Output: OUT STD_LOGIC_VECTOR(7 downto 0));
END Memory;

```

```

ARCHITECTURE memory OF Memory IS
  CONSTANT MAX_ADDR: INTEGER := 4;
  CONSTANT BUS_WIDTH: INTEGER := 8;
  SIGNAL addr: STD_LOGIC_VECTOR(1 downto 0);
  SIGNAL data_in: STD_LOGIC_VECTOR(BUS_WIDTH-1 downto 0);
  SIGNAL CEn, Wn, OEn: STD_LOGIC;
  TYPE MEMORY_ARRAY IS array(0 to MAX_ADDR-1) OF
    STD_LOGIC_VECTOR(BUS_WIDTH-1 downto 0);
  SIGNAL sram: MEMORY_ARRAY;

```

```

BEGIN
  -- port mapping
  addr <= SlideSwitch(9 downto 8);
  data_in <= SlideSwitch(7 downto 0);
  CEn <= PushButton(0);
  Wn <= PushButton(1);
  OEn <= PushButton(2);

```

Declare an 4x8bit RAM

```

PROCESS(ALL)
BEGIN
  -- Memory
  IF(CEn = '0') THEN -- chip enabled
    IF(Wn = '0') THEN -- Write enable
      sram(conv_integer(addr)) <= data_in;
      Output <= (others => '1');
    ELSIF(OEn='0') THEN -- Read enable and output enable
      Output <= sram(conv_integer(addr));
    ELSE
      Output <= (others => '1');
    END IF;
  ELSE
    Output <= (others => '1');
  END IF;
END PROCESS;
END memory;

```

During write operation, output is disabled

Read data from the selected address to the output port

Write input data to the select address

Convert std\_logic\_vector to integer (need to include USE ieee.std\_logic\_unsigned.all; USE ieee.std\_logic\_arith.all; )

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;
USE ieee.std_logic_arith.all;
...
SIGNAL a: STD_LOGIC_VECTOR(7 downto 0);
SIGNAL b: INTEGER RANGE 0 to 255;
a <= conv_std_logic_vector(b, 8);
b <= conv_integer(a);

```

Convert b into a 8-bit std\_logic\_vector

Convert a into an integer.





# Counter Array with Fast Increments

ARCHITECTURE memory OF Memory IS

```
CONSTANT TicksPerMilliSecond: INTEGER := 50000;
```

```
CONSTANT DebounceTime: INTEGER := TicksPerMilliSecond * 5;
```

```
CONSTANT FastCountDelay: INTEGER := TicksPerMilliSecond * 1000;
```

```
CONSTANT FastCountInterval: INTEGER := TicksPerMilliSecond * 100;
```

```
CONSTANT MAX_COUNTER: INTEGER := 16;
```

```
TYPE COUNTER_ARRAY IS array(0 to MAX_COUNTER-1) OF INTEGER RANGE 0 to 99;
```

```
SIGNAL PressedTime: NATURAL := 0;
```

```
SIGNAL cnt: COUNTER_ARRAY;
```

```
SIGNAL cnt_addr: STD_LOGIC_VECTOR(3 downto 0);
```

```
BEGIN
```

```
PROCESS(ALL)
```

```
BEGIN
```

```
-- counters
```

```
IF(clk'EVENT and clk = '1') THEN
```

```
IF(CNTn='0') THEN
```

```
IF(PressedTime < DebounceTime) THEN
```

```
PressedTime <= PressedTime + 1; -- Wait for debounce time
```

```
ELSIF(PressedTime = DebounceTime) THEN
```

```
cnt(conv_integer(cnt_addr)) <= cnt(conv_integer(cnt_addr)) + 1;
```

```
PressedTime <= FastCountInterval; -- Debounce time is reached
```

```
ELSE -- fast and accumulated counting
```

```
PressedTime <= PressedTime + 1; -- Keep accumulating the pressed time
```

```
IF(PressedTime = FastCountDelay+FastCountInterval) THEN -- Reach the fast count point
```

```
cnt(conv_integer(cnt_addr)) <= cnt(conv_integer(cnt_addr)) + 1;
```

```
PressedTime <= FastCountDelay; -- Reset the pressed time to wait for the next delay
```

```
END IF;
```

```
END IF;
```

```
ELSE
```

```
PressedTime <= 0;
```

```
END IF;
```

```
-- reset counter
```

```
IF(cnt(conv_integer(cnt_addr)) > 99) THEN
```

```
cnt(conv_integer(cnt_addr)) <= 0;
```

```
END IF;
```

```
END IF;
```

```
END PROCESS;
```

```
END memory;
```

Define a data structure with 16 integers

Declare an array with 16 counters

Wait until the debouncing time is reached


Wait until the fast increment time is reached






 
# Lab 13

- Design a 4x8bit memory.
  - $addr[1..0]$  is mapped to  $SW[9..8]$  (SlideSwitch);
  - $data\_in[7..0]$  is mapped to  $SW[7..0]$ ;
  - $DQ[7..0]$  is converted into two-hexadecimal digits shown in Hex[1..0] (7-segments).
  - En (chip enable) is mapped to PushButton[0]
  - R/Wn (read/write selection) is mapped to PushButton[1];
  - OEn (or Gn: output enable) is mapped to PushButton[2];
- Design an array of 16 counters with fast increment support
  - Each counter is a two-digit counter that counts from 0 to 99.
  - Each counter is selected by the decoded value of  $SW[3..0]$ .
  - When a counter is selected, its content is shown in Hex[3..2].
  - When PushButton[1] is pushed, the selected counter is advanced by one.
  - If PushButton[1] is pushed for more than one second, the selected counter is advanced by one every 100ms.
- Report:
  - Write down what you have learned from this lab. (實驗心得)




  
# 7-Segment Displays & DE0 – External Clock



Pin number (active-low)

Signal Name	FPGA Pin No.
-------------	--------------

HEX0_D[0]	PIN_E11
HEX0_D[1]	PIN_F11
HEX0_D[2]	PIN_H12
HEX0_D[3]	PIN_H13
HEX0_D[4]	PIN_G12
HEX0_D[5]	PIN_F12
HEX0_D[6]	PIN_F13
HEX0_DP	PIN_D13

HEX1_D[0]	PIN_A13
HEX1_D[1]	PIN_B13
HEX1_D[2]	PIN_C13
HEX1_D[3]	PIN_A14
HEX1_D[4]	PIN_B14
HEX1_D[5]	PIN_E14
HEX1_D[6]	PIN_A15
HEX1_DP	PIN_B15



HEX2_D[0]	PIN_D15
HEX2_D[1]	PIN_A16
HEX2_D[2]	PIN_B16
HEX2_D[3]	PIN_E15
HEX2_D[4]	PIN_A17
HEX2_D[5]	PIN_B17
HEX2_D[6]	PIN_F14
HEX2_DP	PIN_A18

HEX3_D[0]	PIN_B18
HEX3_D[1]	PIN_F15
HEX3_D[2]	PIN_A19
HEX3_D[3]	PIN_B19
HEX3_D[4]	PIN_C19
HEX3_D[5]	PIN_D19
HEX3_D[6]	PIN_G15
HEX3_DP	PIN_G16



# Pushbutton and Slide Switches

Pin number

  

3 Pushbutton switches:  
 Not pressed → Logic High  
 Pressed → Logic Low


Signal Name	FPGA Pin No.
BUTTON [0]	PIN_ H2
BUTTON [1]	PIN_ G3
BUTTON [2]	PIN_ F1

10 Slide switches (Sliders):  
 Up → Logic High  
 Down → Logic

SW[0]	PIN_J6	SW[5]	PIN_J7
SW[1]	PIN_H5	SW[6]	PIN_H7
SW[2]	PIN_H6	SW[7]	PIN_E3
SW[3]	PIN_G4	SW[8]	PIN_E4
SW[4]	PIN_G5	SW[9]	PIN_D2



# LEDs

 

10 LEDs  
 Output high → LED on  
 Output low → LED off

Signal Name	FPGA Pin No.
LEDG[0]	PIN_J1
LEDG[1]	PIN_J2
LEDG[2]	PIN_J3
LEDG[3]	PIN_H1
LEDG[4]	PIN_F2
LEDG[5]	PIN_E1
LEDG[6]	PIN_C1
LEDG[7]	PIN_C2
LEDG[8]	PIN_B2
LEDG[9]	PIN_B1