




Lab 4 – Part 1

- Design a combinational circuit to solve the following question:
 - There are three switches (A, B, and C), one green LED, and one red LED.
 - When the power is on,
 - The red LED is off and the green LED is on when none or one of the switches is on.
 - The red LED is on and the green LED is off when two or three switches are on.



Report 4 – Part 1

- 填寫組員姓名、學號 – 格式不限
 - 使用 AND-OR (SOP)、OR-AND (POS) 或 AOI 電路解決 Part 1 的問題並完成下圖中電路 (並標出所使用的 IC 編號，及導出邏輯線路的過程)。
 - 說明所採用的電路及採用的原因。
 - 實驗心得。

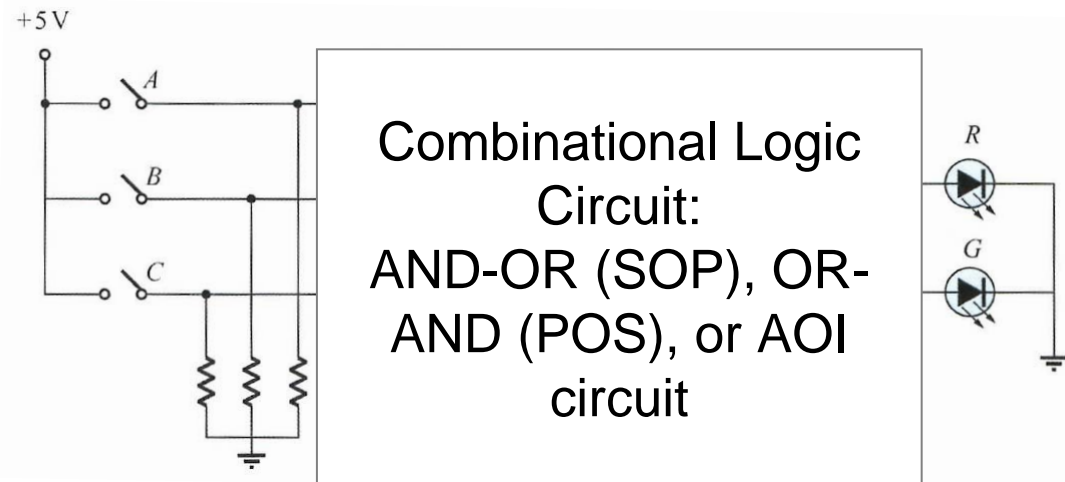




Lab 4 – Part 2

- Design a combinational circuit to solve the following question:
 - There are three switches (A, B, and C) and one LED.
 - When the power is on,
 - The LED is on when any two or more adjacent switches are on at the same time (i.e., A B on, B C on, A B C on).
 - Otherwise, the LED is off.




Report 4 – Part 2

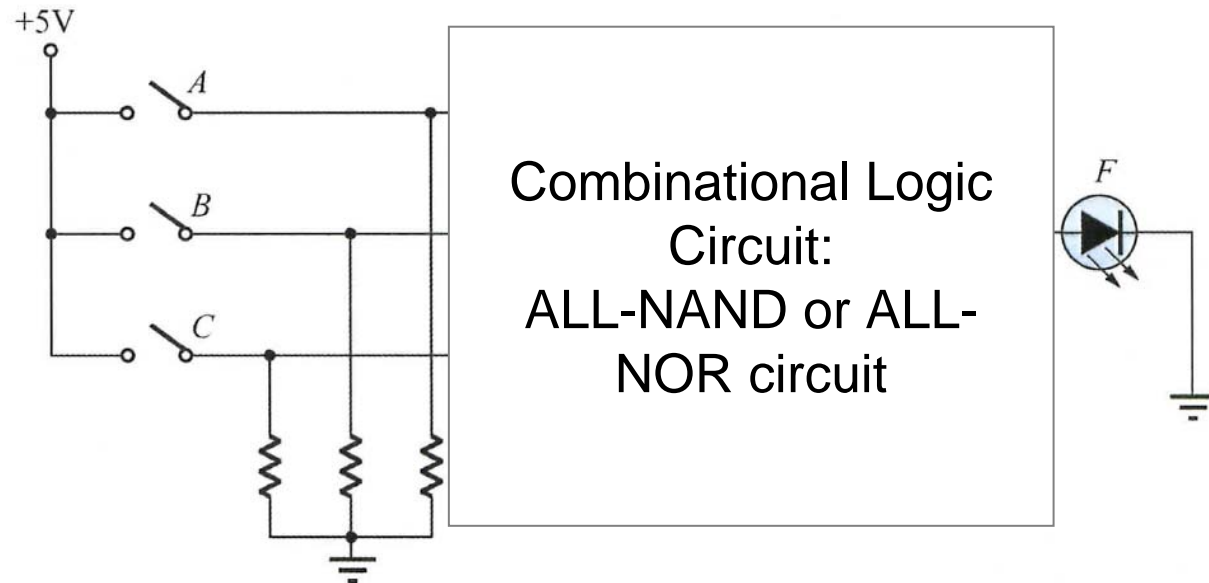- 使用 ALL-NAND 或 ALL-NOR 電路解決 Part 2 的問題並完成下圖中電路 (並標出所使用的 IC 編號，及導出邏輯線路的過程)。
- 說明所採用的電路及採用的原因。
- 實驗心得。







Chip Logic Circuit

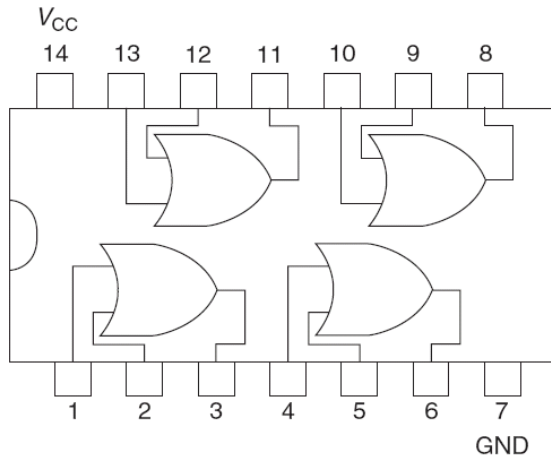

74LS32

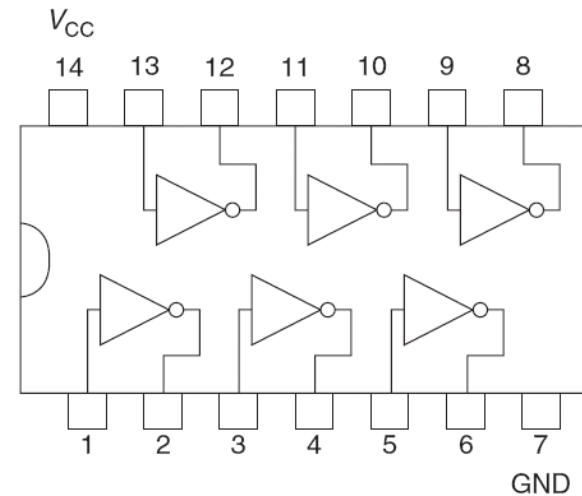


74LS04

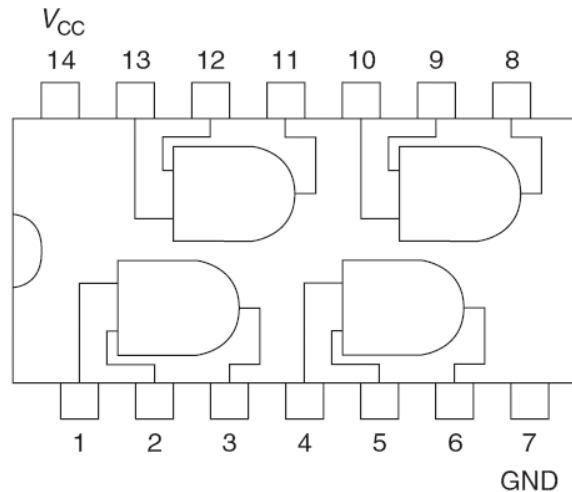


74LS08




Chip Logic Circuit (Cont.)

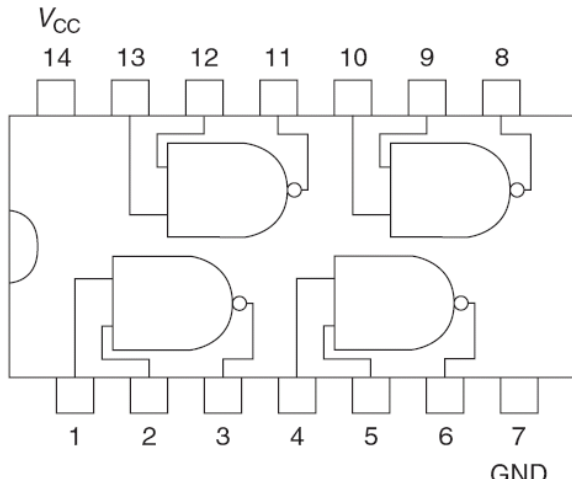

74LS00

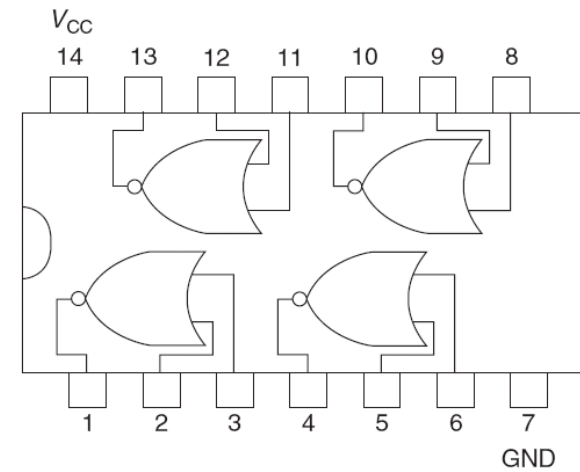

74LS02

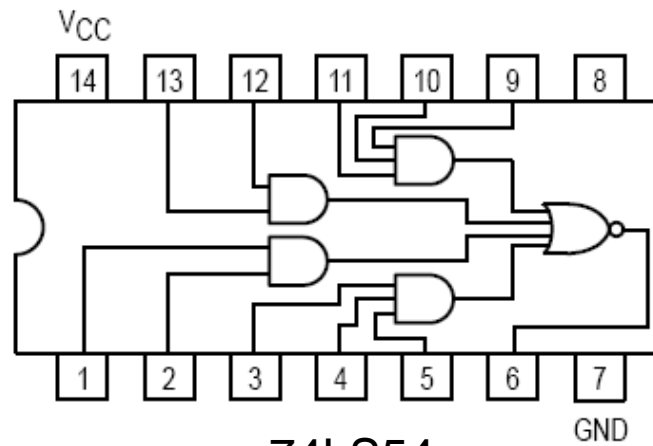

74LS54