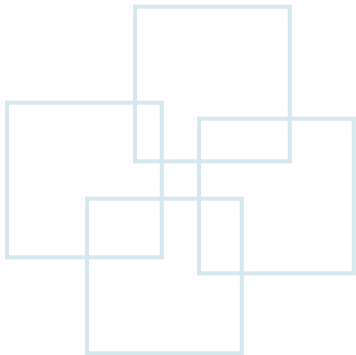


Class 8

MUX / DMUX


and

Full Adder






Multiplexer (MUX)

 

S_1	S_0	Y
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

 

S_1	S_0	Y_3	Y_2	Y_1	Y_0
0	0	D_{03}	D_{02}	D_{01}	D_{00}
0	1	D_{13}	D_{12}	D_{11}	D_{10}
1	0	D_{23}	D_{22}	D_{21}	D_{20}
1	1	D_{33}	D_{32}	D_{31}	D_{30}



Multiplexer (MUX)

```
ENTITY mux4sel IS
  PORT(
    s: IN    BIT_VECTOR (1 downto 0);
    d: IN    BIT_VECTOR (3 downto 0);
    y: OUT   BIT);
END mux4sel;
```


```
ARCHITECTURE a OF mux4sel IS
BEGIN
```

- Selected Signal Assignment

MUX4: WITH s SELECT

```
  y <=      d(0) WHEN "00",
            d(1) WHEN "01",
            d(2) WHEN "10",
            d(3) WHEN "11";
```

```
END a;
```

 

```
ENTITY mux4case IS
```

```
  PORT(
```

```
    d0, d1, d2, d3: IN BIT; -- data inputs
```

```
    s: IN BIT_VECTOR (1 downto 0); -- select inputs
```

```
    y: OUT BIT);
```

```
END mux4case;
```

```
ARCHITECTURE mux4to1 OF mux4case IS
```

```
BEGIN
```

-- Monitor select inputs and execute if they change

```
PROCESS(s)
```

```
BEGIN
```

```
  CASE s IS
```

```
    WHEN "00"      =>    y <= d0;
```

```
    WHEN "01"      =>    y <= d1;
```

```
    WHEN "10"      =>    y <= d2;
```

```
    WHEN "11"      =>    y <= d3;
```

```
    WHEN others    =>    y <= '0';
```




```
  END CASE;
```

```
END PROCESS;
```


```
END mux4to1;
```



Demultiplexer (DMUX)

   

b. Demultiplexer

 

a. Decoder



Demultiplexer (DMUX) (Cont.)

```
ENTITY dmux8 IS
  PORT(
    s: IN    STD_LOGIC_VECTOR(2 downto 0);
    d: IN    STD_LOGIC;
    y: OUT   STD_LOGIC_VECTOR(0 to 7));
END dmux8;
```

```
ARCHITECTURE a OF dmux8 IS
  SIGNAL inputs : STD_LOGIC_VECTOR(3 downto 0);
BEGIN
  inputs <= d & s;
```

```
  WITH inputs SELECT
  y <= "01111111" WHEN "0000",
      "10111111" WHEN "0001",
      "11011111" WHEN "0010",
      "11101111" WHEN "0011",
      "11110111" WHEN "0100",
      "11111011" WHEN "0101",
      "11111101" WHEN "0110",
      "11111110" WHEN "0111",
      "11111111" WHEN others;
```


```
END a;
```

s: selector

d: signal



Half Adder


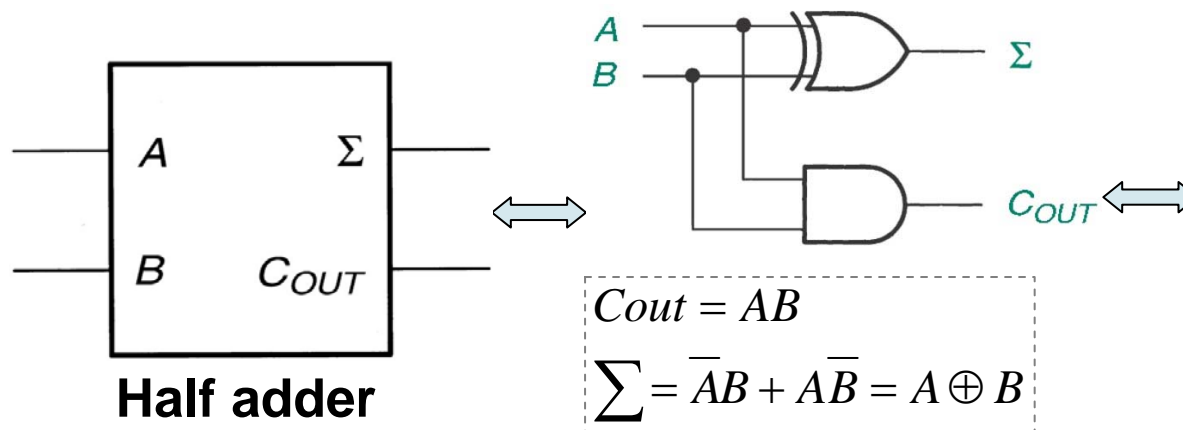


A	B	C _{out}	Σ
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0





Full Adder

A	B	C _{IN}	C _{out}	Σ
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

  

Can't simplify Σ by K-map

  

$$C_{out} = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

$$= (\bar{A}B + A\bar{B})C + AB(\bar{C} + C)$$


$$= (A \oplus B)C + AB$$

$$\Sigma = \bar{A}\bar{B}C + ABC + \bar{A}B\bar{C} + A\bar{B}C$$

$$= (\bar{A}\bar{B} + AB)C + (\bar{A}B + A\bar{B})\bar{C}$$


$$= \overline{(A \oplus B)}C + (A \oplus B)\bar{C}$$

$$= (A \oplus B) \oplus C$$

 



 Parallel Binary Adder (Ripple Carry Binary Adder)




$$A_4A_3A_2A_1 = 1101$$

$$B_4B_3B_2B_1 = 0101$$

$$A + B = 10010$$



Full Adder

 

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
```

```
ENTITY full_add IS
```

```
  PORT(
```

```
    a, b, c_in      : IN      STD_LOGIC;
```

```
    c_out, sum      : OUT     STD_LOGIC);
```

```
END full_add;
```

```
ARCHITECTURE adder OF full_add IS
```

```
  BEGIN
```

```
    c_out <= ((a xor b) and c_in) or (a and b);
```


```
    sum <= (a xor b) xor c_in;
```

```
  END adder;
```

$$\begin{aligned}
 C_{out} &= \bar{A}BC + A\bar{B}C + ABC\bar{C} + ABC \\
 &= (\bar{A}B + A\bar{B})C + AB(\bar{C} + C) \\
 &= (A \oplus B)C + AB \\
 \sum &= \bar{A}\bar{B}C + ABC + \bar{A}B\bar{C} + A\bar{B}\bar{C} \\
 &= (\bar{A}\bar{B} + AB)C + (\bar{A}B + A\bar{B})\bar{C} \\
 &= \overline{(A \oplus B)}C + (A \oplus B)\bar{C} \\
 &= ((A \oplus B) \oplus C)
 \end{aligned}$$



2-Bit Full Adder

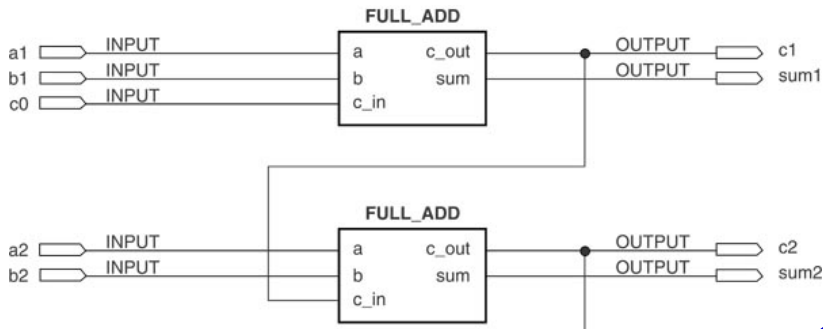

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
```

```
ENTITY add2par IS
PORT(
  c0: IN    STD_LOGIC;
  a, b: IN  STD_LOGIC_VECTOR(2 downto 1);
  c2: OUT   STD_LOGIC;
  sum: OUT  STD_LOGIC_VECTOR(2 downto 1));
END add2par;
```

```
ARCHITECTURE adder OF add2par IS
-- Component declaration
COMPONENT full_add
PORT(
  a, b, c_in: IN    STD_LOGIC;
  c_out, sum: OUT   STD_LOGIC);
END COMPONENT;
-- Define a signal for internal carry bits
SIGNAL c : STD_LOGIC_VECTOR(1 downto 1);
BEGIN
```

```
-- Two Component Instantiation Statements
```

```
adder1: full_add
PORT MAP ( a      => a(1),
           b      => b(1),
           c_in   => c0,
           c_out  => c(1),
           sum    => sum(1));
```

```
adder2: full_add
PORT MAP ( a      => a(2),
           b      => b(2),
           c_in   => c(1),
           c_out  => c2,
           sum    => sum(2));
```

```
END adder;
```

Connect **c_out** of **adder1** to **c_in** of **adder2**

Label is needed

Each component should have different label name

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
```

```
ENTITY full_add IS
PORT(
  a, b, c_in : IN    STD_LOGIC;
  c_out, sum  : OUT   STD_LOGIC);
END full_add;
```

```
ARCHITECTURE adder OF full_add IS
BEGIN
  c_out <= ((a xor b) and c_in) or (a and b);
  sum <= (a xor b) xor c_in;
END adder;
```



2-Bit Full Adder (Cont.)

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY add4gen IS
  PORT(
    c0: IN    STD_LOGIC;
    a, b: IN  STD_LOGIC_VECTOR(2 downto 1);
    c2: OUT   STD_LOGIC;
    sum: OUT  STD_LOGIC_VECTOR(2 downto 1));
END add4gen;

```

```

ARCHITECTURE adder OF add4gen IS
  -- Component declaration
  COMPONENT full_add
    PORT( a, b, c_in: IN    STD_LOGIC;
          c_out, sum: OUT  STD_LOGIC);
  END COMPONENT;
  -- Define a signal for internal carry bits
  SIGNAL c : STD_LOGIC_VECTOR (2 downto 0);
BEGIN
  c(0) <= c0;
  adder1: full_add PORT MAP (a(1), b(1), c0, c(1), sum(1));
  adders:
  FOR i IN 1 to 2 GENERATE
    adder: full_add PORT MAP (a(i), b(i), c(i-1), c(i), sum(i));
  END GENERATE;
  c2 <= c(2);
END adder;

```

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY add2par IS
  PORT(
    c0: IN    STD_LOGIC;
    a, b: IN  STD_LOGIC_VECTOR(2 downto 1);
    c2: OUT   STD_LOGIC;
    sum: OUT  STD_LOGIC_VECTOR(2 downto 1));
END add2par;

```

```

ARCHITECTURE adder OF add2par IS
  -- Component declaration
  COMPONENT full_add
    PORT(
      a, b, c_in: IN    STD_LOGIC;
      c_out, sum: OUT  STD_LOGIC);
  END COMPONENT;
  -- Define a signal for internal carry bits
  SIGNAL c : STD_LOGIC_VECTOR(1 downto 1);
BEGIN
  -- Two Component Instantiation Statements
  adder1: full_add
    PORT MAP ( a    => a(1),
              b    => b(1),
              c_in => c0,
              c_out => c(1),
              sum  => sum(1));
  adder2: full_add
    PORT MAP ( a    => a(2),
              b    => b(2),
              c_in => c(1),
              c_out => c2,
              sum  => sum(2));
END adder;

```



Label is needed



Full Adder with Unspecified Width

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY addxgen IS
  GENERIC (width : INTEGER := 8);
  PORT(
    c0: IN STD_LOGIC;
    a, b: IN STD_LOGIC_VECTOR(width downto 1);
    c_max: OUT STD_LOGIC;
    sum: OUT STD_LOGIC_VECTOR(width downto 1));
END addxgen;

ARCHITECTURE adder OF addxgen IS
  -- Component declaration
  COMPONENT full_add
    PORT(
      a, b, c_in : IN STD_LOGIC;
      c_out, sum: OUT STD_LOGIC);
  END COMPONENT;
  -- Define a signal for internal carry bits
  SIGNAL c : STD_LOGIC_VECTOR (width downto 0);
BEGIN
  c(0) <= c0;
  adders:
  FOR i IN 1 to width GENERATE
    adder: full_add PORT MAP (a(i), b(i), c(i-1), c(i), sum(i));
  END GENERATE;
  c_max <= c(width);
END adder;
  
```

Default value required, but can be redefined.

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY add16gen IS
  PORT(
    c0: IN STD_LOGIC;
    a, b: IN STD_LOGIC_VECTOR(16 downto 1);
    c16: OUT STD_LOGIC;
    sum: OUT STD_LOGIC_VECTOR(16 downto 1));
END add16gen;

ARCHITECTURE adder of add16gen IS
  COMPONENT addxgen
    GENERIC (width : INTEGER);
    PORT(
      c0: IN STD_LOGIC;
      a, b: IN STD_LOGIC_VECTOR(width downto 1);
      c_max: OUT STD_LOGIC;
      sum: OUT STD_LOGIC_VECTOR(width downto 1));
  END COMPONENT;
BEGIN
  add16 : addxgen
  GENERIC MAP(width => 16)
  PORT MAP(c0, a, b, c16, sum);
END adder;
  
```

Included components should be in the same Quartus project as well.

“width” is specified in GENERIC MAP



The Procedure to Import VHDL Code to Block Diagram/Schematic File

- The procedure to import a VHDL full-adder to a .bdf file to construct a four-bit full adder:
 - 1. Create a quartus project with entity name “adder”
 - 2. Create a new `full_add.vhd` file and save it as a `full_add.bsf` file. (File→Create/Update→Create Symbol File...)
 - 3. Create a new `adder.bdf` file (the file name is its entity name)
 - 4. Include `full_add.bsf` file as a component into `adder.bdf`
 - 5. Pin assignment to complete the design


```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;


ENTITY full_add IS
  PORT(
    a, b, c_in : IN          STD_LOGIC;
    c_out, sum : OUT         STD_LOGIC);
END full_add;

ARCHITECTURE adder OF full_add IS
BEGIN
  c_out <= ((a xor b) and c_in) or (a and b);
  sum <= (a xor b) xor c_in;
END adder;
  
```

full_add.vhd

 

full_add.bsf

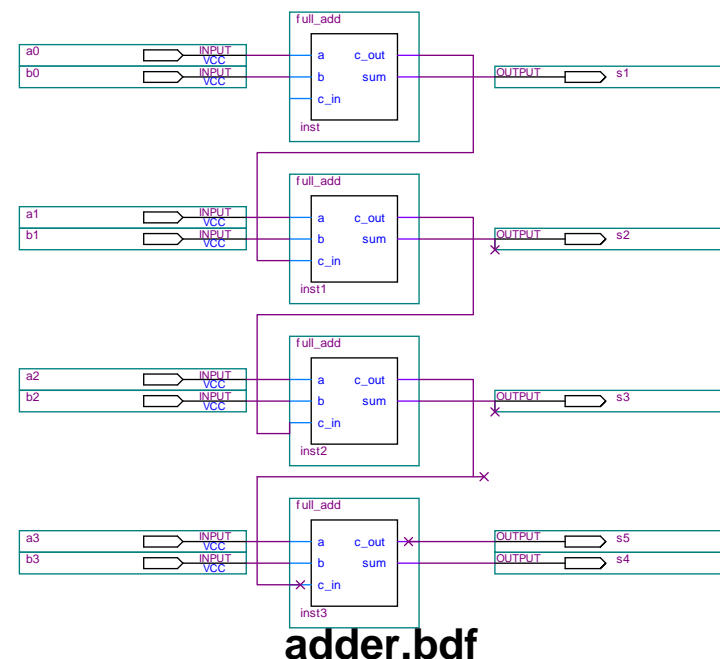

adder.bdf




Lab 8

 • Part 1: Design a MUX/DMUX

- Use Button2-Button0 as the selectors to decide which slide switch among SW7-SW0 is selected to show its status on its corresponding LED. The LEDs that are not selected should be turned off. For example:



- When Button2 is pushed, the status of SW4 is shown on LEDG4.
- When Button2 and Button0 are both pushed, the status of SW5 is shown on LEDG5.



  • Part 2: Full adder

- Implement a 4-bit full adder:

- SW7-4 is the first 4-bit operand, and SW3-0 is the second 4-bit operand.
- Please show the result on LEDs, where LEDG4 is the carry of the MSB bit, and LEDG3-0 are $\sum 3-0$, respectively.
 - LED is on when the corresponding \sum bit is 1.





• Report:

- Write down what you have learned from this lab. (實驗心得)



Pushbutton and Slide Switches

Pin number

  

3 Pushbutton switches:
 Not pressed → Logic High
 Pressed → Logic Low


Signal Name	FPGA Pin No.
BUTTON [0]	PIN_ H2
BUTTON [1]	PIN_ G3
BUTTON [2]	PIN_ F1

10 Slide switches (Sliders):
 Up → Logic High
 Down → Logic

SW[0]	PIN_ J6	SW[5]	PIN_ J7
SW[1]	PIN_ H5	SW[6]	PIN_ H7
SW[2]	PIN_ H6	SW[7]	PIN_ E3
SW[3]	PIN_ G4	SW[8]	PIN_ E4
SW[4]	PIN_ G5	SW[9]	PIN_ D2



LEDs

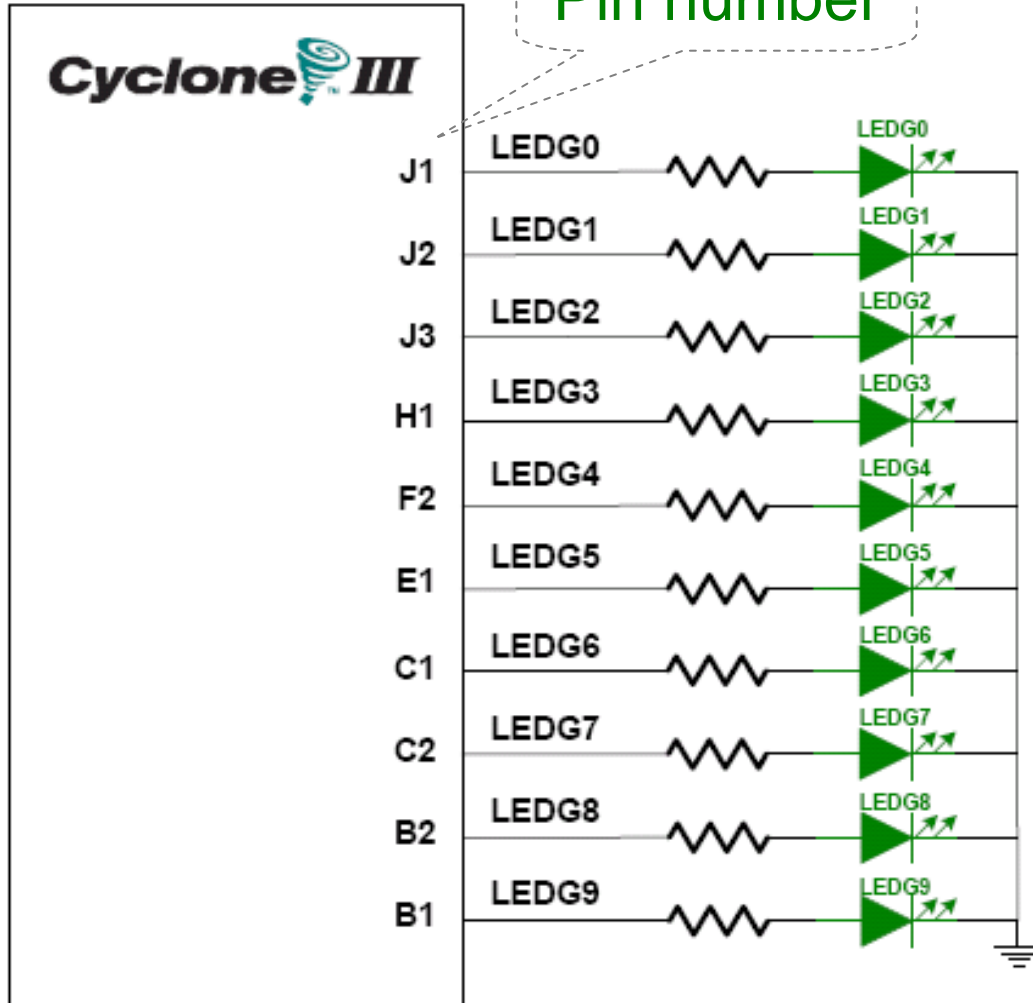


10 LEDs
 Output high → LED on
 Output low → LED off

Signal Name	FPGA Pin No.
LEDG[0]	PIN_J1
LEDG[1]	PIN_J2
LEDG[2]	PIN_J3
LEDG[3]	PIN_H1
LEDG[4]	PIN_F2
LEDG[5]	PIN_E1
LEDG[6]	PIN_C1
LEDG[7]	PIN_C2
LEDG[8]	PIN_B2
LEDG[9]	PIN_B1



7-Segment Displays

Pin number (active-low)

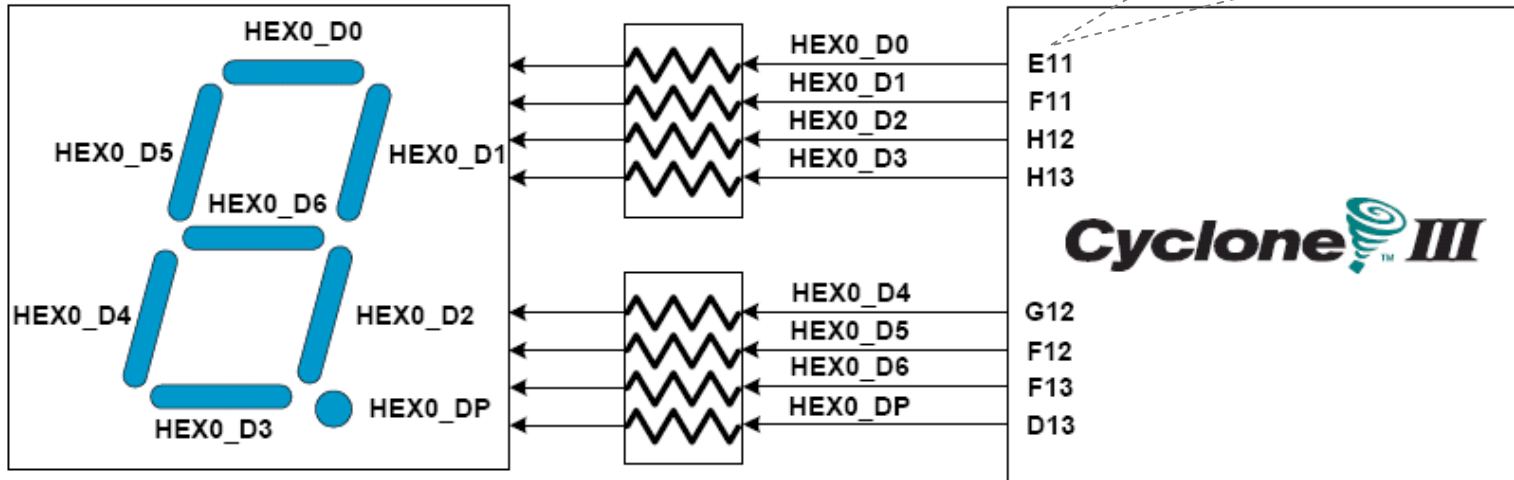

Signal Name	FPGA Pin No.
HEX0_D[0]	PIN_E11
HEX0_D[1]	PIN_F11
HEX0_D[2]	PIN_H12
HEX0_D[3]	PIN_H13
HEX0_D[4]	PIN_G12
HEX0_D[5]	PIN_F12
HEX0_D[6]	PIN_F13
HEX0_DP	PIN_D13

HEX1_D[0]	PIN_A13
HEX1_D[1]	PIN_B13
HEX1_D[2]	PIN_C13
HEX1_D[3]	PIN_A14
HEX1_D[4]	PIN_B14
HEX1_D[5]	PIN_E14
HEX1_D[6]	PIN_A15
HEX1_DP	PIN_B15

HEX2_D[0]	PIN_D15
HEX2_D[1]	PIN_A16
HEX2_D[2]	PIN_B16
HEX2_D[3]	PIN_E15
HEX2_D[4]	PIN_A17
HEX2_D[5]	PIN_B17
HEX2_D[6]	PIN_F14
HEX2_DP	PIN_A18

HEX3_D[0]	PIN_B18
HEX3_D[1]	PIN_F15
HEX3_D[2]	PIN_A19
HEX3_D[3]	PIN_B19
HEX3_D[4]	PIN_C19
HEX3_D[5]	PIN_D19
HEX3_D[6]	PIN_G15
HEX3_DP	PIN_G16